

Contents

Preface	ix
Acknowledgements	xi
1. Essential Electronics	1
1.1: Current	2
1.2: Voltage	5
1.3: Power	6
1.4: Signals and Averages	7
1.4.1: Mean Average	7
1.4.2: Rectified Average	8
1.4.3: RMS Average	8
1.5: Complex Numbers	9
1.5.1: Complex Arithmetic	11
1.6: Phasors	12
1.7: Fourier's Theorem	14
1.8: Resistance and Ohm's Law	17
1.8.1: Resistance in Series and Parallel	17
1.9: Capacitance	18
1.9.1: Capacitive Reactance	21
1.9.2: Capacitors in Series and Parallel	22
1.10: Inductance	22
1.10.1: Inductive Reactance	24
1.10.2: Inductors in Series and Parallel	24
1.11: Impedance	25
1.12: Kirchoff's Voltage Law	27
1.13: Kirchoff's Current Law	27
1.14: Sources	28
1.14.1: Voltage and Current Sources	28
1.14.2: Dependent Sources	29
1.15: Thévenin's Theorem	30
1.16: Norton's Theorem	31
1.17: Potential Dividers	31
1.18: Current Dividers	33
1.19: The Principle of Superposition	34
1.20: Linear Circuit Analysis	35
1.21: Resonance	37
1.22: Filters	39
1.22.1: Bode Plots	45
1.22.2: Phase Delay	47
1.23: Step Response	50
1.24: Negative Feedback	53
1.24.1: The Universal Feedback Equation	54

1.24.2: Virtual Earth	57
1.24.3: General Properties of Negative Feedback	58
1.24.4: Stability	60
2. Practical Components	64
2.1: Resistors	64
2.1.1: Resistance	64
2.1.2: Tolerance	65
2.1.3: Power Rating	65
2.1.4: Voltage Rating	65
2.1.5: Excess Noise	66
2.1.6: Temperature Coefficient	66
2.1.7: Parasitics	66
2.1.8: Metal Film	67
2.1.9: Metal Oxide	67
2.1.10: Carbon Film	67
2.1.11: Carbon Composition	68
2.1.12: Wirewound	69
2.1.13: Fusible / Flameproof Resistors	70
2.1.14: Potentiometers	70
2.2: Capacitors	71
2.2.1: Capacitance	72
2.2.2: Tolerance	72
2.2.3: Voltage Rating	73
2.2.4: Leakage	73
2.2.5: ESR	73
2.2.6: Loss Tangent / Dissipation Factor	73
2.2.7: Ripple Current	74
2.2.8: Dielectric Absorption	75
2.2.9: Parasitics	75
2.2.10: Air	76
2.2.11: Silvered Mica	76
2.2.12: Ceramic	76
2.2.13: Plastic / Film	78
2.2.14: Aluminium Electrolytic	80
2.2.15: Tantalum	86
2.3: Inductors	86
2.3.1: Distortion	87
2.3.2: Parasitics	89
2.3.3: Ferrite Beads	89
2.4: Power Transformers	89
2.4.1: VA (Power) Rating	90
2.4.2: Regulation	91
2.4.3: Phasing	91

2.5: Small-Signal Transformers	92
2.5.1: Turns and Impedance Ratios	93
2.5.2: Source and Load Impedances	93
2.5.3: Parasitics	94
2.5.4: Distortion	96
2.6: Valves	97
2.6.1: The Anode	98
2.6.2: The Grids	99
2.6.3: The Cathode	100
2.6.4: The Heater	102
2.6.5: Electrostatic Shields	103
2.6.6: The Getter	103
2.6.7: The Mica Spacers	104
2.6.8: Variable-Mu / Remote Cut-off Valves	104
2.6.9: Valve Ratings	104
2.6.10: Anode Voltage Rating	105
2.6.11: Anode Dissipation Rating	105
2.6.12: Heater Voltage and Current Rating	106
2.6.13: Heater-Cathode Voltage Rating	108
2.6.14: Heater-Cathode Resistance Rating	109
2.6.15: Grid Voltage Ratings	109
2.6.16: Grid Dissipation Ratings	110
2.6.17: Grid Current	110
2.6.18: Grid-Leak Resistance Rating	112

3. Fundamentals of Amplification **113**

3.1: Basic Theory of Valves	113
3.1.1: Valve Diodes	114
3.1.2: Triodes	115
3.2: The Valve Constants	117
3.2.1: Anode Resistance, r_a	118
3.2.2: Amplification Factor, μ	119
3.2.3: Transconductance, g_m	120
3.3: Amplification	121
3.3.1: The Load Line	121
3.3.2: Biasing	123
3.3.3: The Cathode Load Line	125
3.3.4: Resistor Ratings	127
3.3.5: The Safe Operating Area	127
3.4: Distortion and the Transfer Function	129
3.4.1: Harmonic Distortion	130
3.4.2: Intermodulation Distortion	132
3.5: Clipping and Headroom	133
3.6: The Effect of Load on Distortion	136
3.6.1: The Golden Ratio	137

3.6.2: The AC Load Line	138
3.7: The Cathode Bypass Capacitor	140
3.8: Equivalent Circuits	143
3.8.1: Gain Equations	144
3.9: Impedance Matching and Bridging	146
3.9.1: Output Impedance	147
3.9.2: Input Impedance and the Miller Effect	149
3.10: Oscillation and Stoppers	150
3.11: Slew Rate and Reactive Loads	152
3.12: Power Supply Rejection Ratio, PSRR	156
3.13: Coupling	158
3.13.1: Blocking Distortion	159
3.13.2: Minimising Blocking Distortion	161
3.13.3: DC Coupling	162
3.13.4: Grid-Cathode Arc Protection	163
3.13.5: Level Shifting	164
4. The Small-Signal Pentode	166
4.1: The Screen Grid	166
4.1.1: Secondary Emission	167
4.1.2: The Suppressor Grid	167
4.2: The Effect of Screen Voltage	168
4.3: The Effect of Screen Current	170
4.3.1: The Anode/Screen Current Ratio	171
4.4: Deriving Grid Curves for any Screen Voltage	172
4.5: Basic Design Equations	173
4.5.1: The Effect of Screen and Cathode Bypassing	175
4.6: A Traditional Pentode Gain Stage	176
4.6.1: The Effect of Cathode Degeneration	178
4.6.2: The Effect of Screen Degeneration	179
4.6.3: The Effect of Load on Distortion	180
4.7: Designing a Pentode Stage the Easy Way	182
4.8: Pentodes Connected as Triodes	185
4.8.1: Low-Capacitance Mode	186
5. Noise, Hum and Microphony	188
5.1: Noise	188
5.1.1: Johnson or Thermal Noise	189
5.1.2: Shot Noise	190
5.1.3: Flicker or Excess Noise	191
5.1.4: Adding Noise Sources	192
5.1.5: Equivalent Input Noise	193
5.1.6: Noise Bandwidth	194
5.1.7: Noise Spectral Density	195
5.1.8: Noise Weighting	197

5.2: Noise in Resistors	198
5.3: Noise in Triodes	199
5.3.1: EIN Spectral Density	201
5.3.2: Total EIN	203
5.4: Noise in Pentodes	206
5.5: Noise in Bipolar Transistors	208
5.6: Noise in Field Effect Transistors	209
5.7: Noise in Diodes	210
5.8: Noise Calculations	211
5.8.1: Triode Gain Stage	211
5.8.2: Parallel Valves	214
5.8.3: Principles of Low-Noise Design	215
5.9: Hum	215
5.9.1: Electric Fields	216
5.9.2: Magnetic Fields	216
5.9.3: Transformers and Hum	216
5.9.4: Electric Shielding	217
5.9.5: Magnetic Shielding	218
5.9.6: Lead Dress	218
5.10: Microphony	220
6. Advancements in Amplification	221
6.1: Current-Source Loading	221
6.1.1: Triode Current Source	222
6.1.2: Simple BJT Current Source	224
6.1.3: Cascode BJT Current Source	226
6.1.4: FET Current Sources	228
6.2: Valve Distortion Measurements	230
6.2.1: ECC81 / 12AT7	232
6.2.2: ECC82 / 12AU7	234
6.2.3: ECC83 / 12AX7	236
6.2.4: ECC84 / 6CW7	237
6.2.5: ECC88 / 6DJ8	239
6.2.6: 6Ж52Π / 6J52P	240
6.2.7: 6SN7GT	241
6.2.8: Summary	242
6.3: Diode Biasing	243
7. The Cathode Follower	247
7.1: Design Equations	247
7.1.1: Gain	248
7.1.2: Input Impedance	249
7.1.3: Output Impedance	251
7.1.4: PSRR	253

7.2: Noise	254
7.3: Oscillation and Stoppers	254
7.4: Anode Characteristics	256
7.4.1: Using the New Anode Characteristics	257
7.5: Cathode Bias	259
7.6: Fixed Bias	261
7.7: DC Coupling	264
7.8: Distortion Cancellation	266
7.9: The Bootstrapped Pair	267
7.10: The Constant-Current-Draw Amplifier	270
7.11: Transistor Followers	273
7.12: Active Loading	274
7.13: Output Voltage Limiting	275
7.14: Compound Cathode Followers	278
7.14.1: Feed-forward Noise Cancellation	279
7.14.2: The White Cathode Follower	281
7.14.3: A Transformerless Headphone Driver	284
8. Compound Amplifiers	288
8.1: Totem-Pole Gain Stages	288
8.1.1: The Half- μ Stage	288
8.1.2: The SRPP	293
8.1.3: The μ -Follower	299
8.1.4: The Cascode	304
8.2: The Cathode-Coupled Amplifier	309
9. Controls	315
9.1: Source Selection	315
9.2: Volume Control	316
9.2.1: Potentiometers	317
9.2.2: Stepped Attenuators	319
9.2.3: Relay Attenuators	321
9.3: Balance Control	321
9.4: Tone Controls	324
9.4.1: Passive James/Baxandall Tone Controls	325
9.4.2: Passive Tilt Control	328
9.4.3: Active James/Baxandall Tone Controls	330
9.4.4: Active Tilt Control	333
10. The Phono Stage	335
10.1: RIAA Equalisation	335
10.1.1: The IEC Amendment	336
10.1.2: The Neumann Fallacy	337

10.2: Phono Stage Design	338
10.2.1: Active Equalisation	339
10.2.2: RIAA Accuracy	340
10.3: Realising Passive Equalisation	341
10.3.1: An Inverse RIAA Filter	344
10.4: The Input Stage	345
10.4.1: Moving-Magnet Pickup Cartridges	345
10.4.2: Valve Choice	346
10.5: Moving-Coil Pickup Cartridges	348
10.5.1: Moving-Coil Input Transformers	349
10.5.2: Active Moving-Coil Head Amplifiers	350
10.6: A Moving-Magnet Phono Design Example	353
10.6.1: The Input Stage	354
10.6.2: Fleshing-Out The Design	355
10.6.3: The Second Stage	356
10.6.4: The Output Stage	357
10.6.5: The Power Supply	359
10.6.6: Measured Performance	361
11. Power Supplies	364
11.1: Essentials of Rectification	365
11.1.1: Average DC Output Voltage	366
11.1.2: Ripple Voltage and Reservoir Capacitance	369
11.1.3: Ripple Current	370
11.1.4: Power Factor and VA Rating	372
11.1.5: Diode Ratings	373
11.1.6: Switching Noise and Fast Rectifiers	374
11.2: Voltage Multipliers	377
11.3: Valve Rectifiers	379
11.3.1: Electrical Ratings	380
11.3.2: Voltage Drop	382
11.3.3: Heater Supply	382
11.3.4: Hot Switching and Inrush Current	383
11.4: Choke-Input Rectifiers	383
11.4.1: Design Calculations	384
11.5: Power Supply Refinements	387
11.5.1: Inrush Current Limiting	387
11.5.2: Fuses	388
11.5.3: Switches and Switching	389
11.5.4: Transient Suppression	390
11.5.5: EMI Filtering	391
11.5.6: Bleeder Resistor	391
11.6: Smoothing, Bypassing and Decoupling	392
11.6.1: Smoothing	392
11.6.2: Bypassing	394

11.6.3: Decoupling	395
11.6.4: LC Versus RC Filters	396
11.6.5: The Gyrator or Simulated Inductor	398
11.6.6: The Capacitor Multiplier	399
11.7: Voltage Regulation	400
11.7.1: Linear Regulator ICs	400
11.7.2: Adjustable Regulators	402
11.7.3: Low-Dropout Regulators	403
11.7.4: Switching Regulators	404
11.7.5: High-Voltage Regulators	405
11.7.6: Heatsinking	409
11.8: Heater Supplies	412
11.8.1: Rectifier-Induced Hum	412
11.8.2: Electrical Heater Balancing	413
11.8.3: Heater Elevation	414
11.8.4: Common-Mode Noise	415
11.8.5: DC Heater Supplies	416
11.8.6: Accommodating Different Heaters	418
11.9: Back-to-Back Transformers	420
11.10: Reducing Primary Voltage	421
11.11: Transformerless Supplies	422
11.12: External Power Supplies	423