

Contents

Preface	vii
Acknowledgements	viii

1. Mains Power and Transformers	1
1.1: Mains Electricity	2
1.1.1: Mains Distribution	2
1.2: Mains Appliance Wiring	3
1.2.1: Earthing and Safety	4
1.3: Basic Electromagnetics	6
1.3.1: The Ohm's Law of Magnetism	6
1.3.2: Faraday's Law of Inductance	8
1.4: Basic Transformer Theory	9
1.4.1: Phasor Diagrams	11
1.4.2: Transformer Losses	13
1.4.3: The BH Curve	14
1.4.4: Saturation	17
1.5: Transformers and Their Ratings	19
1.5.1: VA (Power) Rating	20
1.5.2: Regulation	21
1.5.3: Phasing	21
1.6: Testing Power Transformers	22
1.6.1: Voltages	22
1.6.2: Phase	23
1.6.3: Power and Current Capability	24

2. Rectification	27
2.1: Essentials of Rectification	27
2.1.1: Half-Wave Rectification	27
2.1.2: Full-Wave Rectification	28
2.1.3: The Reservoir Capacitor	29
2.2: Estimating Idealised Rectifier Performance	30
2.2.1: Ripple Voltage	30
2.2.2: Ripple Current	33
2.3: Estimating Practical Rectifier Performance	36
2.3.1: Average DC Output Voltage	36
2.3.2: Ripple Voltage and Reservoir Capacitance	39
2.3.3: Ripple Current	40
2.3.4: Power Factor and VA Rating	42
2.3.5: Capacitor Voltage Sharing	44
2.4: Diode Ratings	44
2.4.1: Voltage Rating	45
2.4.2: Current Rating	47
2.4.3: Switching Noise and Fast Rectifiers	47

2.5: Some Rectifier Circuit Arrangements	50
2.6: Valve Rectifiers	53
2.6.1: Electrical Ratings	53
2.6.2: Voltage Drop	56
2.6.3: Heater Supply	56
2.6.4: Hot Switching and Inrush Current	57
2.6.5: Hybrid Rectifiers	58
2.6.6: Load Regulation and Sag	58
2.6.7: Gas Rectifier Tubes	60
2.7: Choke-Input Rectifiers	60
2.7.1: Design Calculations	61
3. Voltage Multipliers	65
3.1: Half-Wave Voltage Doubler	65
3.2: Full-Wave Voltage Doubler	67
3.2.1: Bipolar Supply	68
3.2.2: Switchable Doubling	69
3.2.3: Tweakable Output Voltage	69
3.3: Ladder / Greinacher Multiplier	70
3.3.1: Full-Wave Ladder Multiplier	71
3.3.2: Two-Phase Ladder Multiplier	72
3.4: Capacitor-Coupled Bridge Rectifier	74
3.5: Disparate HT Voltages	76
3.6: Some Practical Multiplier Circuits	77
3.6.1: Voltage Doubler	78
3.6.2: Voltage Quadrupler	78
3.6.3: Voltage Sextupler	78
3.6.4: Voltage Octupler	79
3.6.5: Power Supply for a Circotron	80
3.7: Multiplier Cheat Sheets	80
3.7.1: Full-Wave Voltage Doubler	80
3.7.2: Full-Wave Voltage Quadrupler	81
3.7.3: Full-Wave Voltage Sextupler	81
4. Smoothing Filters	83
4.1: Smoothing, Bypassing, and Decoupling	83
4.1.1: Smoothing	84
4.1.2: Bypassing	86
4.1.3: Decoupling	87
4.1.4: High-Frequency Performance	89
4.2: RC Smoothing	90
4.2.1: RC Filter Chains	91
4.2.2: Tuned RC Filters	92
4.3: LC Smoothing	94
4.3.1: Avoiding Resonance in LC Filters	95
4.3.2: Tuned LC Filters	97

4.3.3: Measuring Smoothing Chokes	99
4.3.4: Power Transformers as Chokes	101
4.4: Active Smoothing	102
4.4.1: The Capacitor Multiplier	102
4.4.2: The Gyrator or Simulated Inductor	106
5. Fusing, Switching, and Other Refinements	108
5.1: Fuses	108
5.1.1: Current Rating	109
5.1.2: Voltage Rating	110
5.1.3: Primary Fusing	110
5.1.4: Secondary Fusing	111
5.1.5: Resettable Fuses	113
5.1.6: Fuse Annunciation	114
5.2: Switches and Switching	114
5.2.1: Primary Switching	114
5.2.2: Secondary Switching	115
5.3: Standby Switching	115
5.3.1: Standby-Switch Origins	116
5.3.2: Cathode Stripping	118
5.3.3: Cathode Poisoning	119
5.3.4: Least-Worst Standby Switches	120
5.3.5: Automatic Delay	122
5.4: More Power Supply Refinements	125
5.4.1: Inrush Current Limiting	125
5.4.2: Transient Suppression	126
5.4.3: EMI Filtering	126
5.4.4: Bleeder Resistor	127
6. Shunt Stabilisers and Regulators	128
6.1: Shunt Voltage Regulation	128
6.1.1: Principles and Shunt Regulation	129
6.1.2: Line and Load Regulation	130
6.2: Passive Shunt Regulators	130
6.2.1: Zener Diodes	131
6.2.2: Internal Dynamic Resistance	132
6.2.3: Noise in Zener Diodes	133
6.2.4: Amplified Zener	134
6.3: Glow-Discharge Devices	135
6.3.1: Gas Stabiliser Tubes	136
6.3.2: Neon Lamps	138
6.4: Shunt Stabilisers and Load Lines	139
6.5: Feedforward Shunt Valve Regulators	141
6.5.1: Feedforward Ripple Suppressor	141
6.5.2: King Regulator	144
6.6: Feedback Shunt Valve Regulators	145

6.6.1: Feedback Ripple Suppressor	146
6.6.2: Back-Biased Ripple Suppressor	147
6.6.3: Mixed-Moded Ripple Suppressor	148
6.6.4: King-Type Feedback Shunt Regulator	149
6.6.5: Enhanced King-Type Regulators	150
6.6.6: Cascode Ripple Suppressor	152
6.6.7: Janus Ripple Suppressor	153
6.6.8: Culsans Ripple Suppressor	155
6.7: Transistor Shunt Regulators	155
6.7.1: King-Type Regulator	155
6.7.2: Cascode Regulator	156
6.7.3: King-Type Regulator with Amplified Zener	157
6.7.4: Amplified Zener Cascode	158
6.8: Constant-Current-Enhanced Shunt Regulation	159

7. Series Stabilisers and Regulators **162**

7.1: Series Regulation	162
7.1.1: Principles of Feedback Regulation	162
7.1.2: Classic Topologies	163
7.1.3: Voltage Sharing	165
7.1.4: BJTs vs. MOSFETs	165
7.2: Current Sensing and Limiting	167
7.2.1: Constant-Current Limiting	168
7.2.2: Foldback Current Limiting	169
7.2.3: Overload Trip	171
7.2.4: High Side vs. Low Side	171
7.3: Cooling and Heat Sinking	173
7.3.1: Thermal Calculations	173
7.3.2: Testing Heatsinks	175
7.3.3: Some Practical Advice	176
7.3.4: Thermostatic Switches	178
7.3.5: Dissipation in Bench Power Supplies	178
7.4: Three-Terminal Regulator ICs	181
7.4.1: Adjustable Regulator ICs	183
7.4.2: Low-Dropout Regulators	185
7.4.3: High-Voltage Regulator ICs	185
7.5: Switching Regulators and Converters	186
7.5.1: 555 Boost Converter	187
7.5.2: 40106 Voltage Multipliers	188
7.6: HT Voltage Reducers	190
7.6.1: Voltage Follower	190
7.6.2: Conduction Angle Regulator	192
7.6.3: Optical HT Control	194
7.7: HT Series Regulators	196
7.7.1: Zener Follower	196
7.7.2: Classic Valve Regulator	197

7.7.3: Classic Transistor Regulator	201
7.7.4: Hybrid Maida Regulator	202
7.7.5: Maida Regulator	203
7.7.6: Floating Error Amp (T-Reg)	207
7.7.7: Opto-Coupler Regulator	209
8. Valve Bias Supplies	210
8.1: Bias Voltage Stabilisation and Regulation	210
8.2: Bias Adjustment and Balancing	210
8.2.1: Bias Voltage Adjustment	212
8.2.2: Bias Balance Adjustment	213
8.3: Nuisance Fuse Blowing	215
8.4: Sourcing Bias Voltage	215
8.4.1: Half-Wave Bias Supply	217
8.4.2: Full-Wave Bias Supply	219
8.4.3: Capacitor-Coupled Bias Supply (No Centre Tap)	220
8.4.4: Capacitor-Coupled, Full-Wave Bias Supply	221
8.4.5: Auxiliary Winding Bias Supply	222
8.4.6: Back Biasing	223
9. Valve Heater Supplies	226
9.1: Valve Heaters	226
9.1.1: Heater Voltage and Current Rating	227
9.1.2: Heater-Cathode Voltage Rating	229
9.1.3: Heater-Cathode Resistance Rating	230
9.2: AC Heater Supplies	231
9.2.1: Series and Parallel Combinations	232
9.2.2: Dropping Heater Voltage	233
9.2.3: Wattless Dropper for Series Heaters	234
9.3: Hum	235
9.3.1: Electric Fields	235
9.3.2: Magnetic Fields	236
9.3.3: Lead Dress	237
9.3.4: Rectifier-Induced Heater Hum	238
9.3.5: Electrical Heater Balancing	239
9.3.6: Heater Elevation	240
9.4: DC Heater Supplies	241
9.4.1: Simple DC Heater Supplies	242
9.4.2: Common-Mode Filtering	243
9.4.3: The Free Lunch	243
9.4.4: Linear Regulators	245
9.4.5: Switching Regulators	248
9.4.6: Constant-Current Regulators	250
9.5: Substituting Different Valves	251
9.6: Directly Heated Valves	254

10. Voltage Control	258
10.1: Primary-Side Voltage Control	258
10.2: Secondary-Side Voltage Control	259
10.2.1: Zener Diodes	260
10.3: Scaling Output Power in Guitar Amps	262
10.3.1: Power and Perceived Loudness	262
10.3.2: Simple Power Reduction	265
10.3.3: Proportional Voltage Scaling	265
10.3.4: Power Adjustment Topologies	268
10.3.5: Design Considerations	270
10.3.6: Power Adjustment for Low-Power Amps	272
10.3.7: Power Adjustment for High-Power Amps	273
10.3.8: Screen Tracking	275
10.3.9: Bias Tracking	276
10.4: Cheap and Dirty Power Supplies	279
10.4.1: Back-to-Back Transformers	279
10.4.2: Dual-Primary Misuse	280
10.5: External Power Supplies	281